

Car Parking System in VHDL

A Finite State Machine Approach

AUTHOR

Philippe Velha

1 Introduction

This laboratory aims at the complete VHDL implementation of an automated car parking system. The work is in 2 phases. The first phase looks at a simplified car park where you will have to create the different parts of the design and finally write the VHDL code. All the work will be performed in simulation only so the sensors are considered perfect. The design exercises on key concepts in digital design including:

- Finite State Machine (FSM) design
- Sequential and combinational logic
- Sensor-based control systems
- Password validation
- Visual feedback using LEDs and 7-segment displays (from a simulation point of view)

1.1 System Overview

The car parking system controls access to a parking facility with physical barriers using:

- **Two sensors:** Front sensor (detects approaching cars) and back sensor (detects cars passing through)
- **Password input:** Two 2-bit password inputs that must match a predefined code. The user has 4 buttons labelled A, B, C and D corresponding to the code '00', '01', '10' and '11' respectively (in practice you can see it as a single 4 bit password).
- **Visual feedback:** Red and green LEDs, plus two 7-segment displays
- **Gate control logic:** Implemented as a finite state machine

2 Architecture Analysis

2.1 Entity Declaration

This declaration is mandatory as you will be asked to pass it to other groups!

```
entity Car_Parking_System_VHDL is
port
(
  clk, reset_n: in std_logic;
  front_sensor, back_sensor: in std_logic;
  password_1, password_2: in std_logic_vector(1 downto 0);
  GREEN_LED, RED_LED: out std_logic;
  HEX_1, HEX_2: out std_logic_vector(6 downto 0)
);
end Car_Parking_System_VHDL;
```

2.1.1 Port Descriptions

Port	Direction	Type	Description
clk	Input	std_logic	System clock
reset_n	Input	std_logic	Active-low asynchronous reset
front_sensor	Input	std_logic	Detects car at entrance
back_sensor	Input	std_logic	Detects car passing gate
password_1	Input	2-bit vector	First password digit
password_2	Input	2-bit vector	Second password digit
GREEN_LED	Output	std_logic	Success indicator
RED_LED	Output	std_logic	Wait/error indicator
HEX_1	Output	7-bit vector	First 7-segment display
HEX_2	Output	7-bit vector	Second 7-segment display

Note: The correct password is: `password_1 = "01"` and `password_2 = "10"`

This design uses two separate 2-bit inputs that together form a 4-bit password ("0110" when concatenated). While functional, a **better design approach** would be to use a single 4-bit password input:

```
password: in std_logic_vector(3 downto 0); -- Single 4-bit password
```

Note: As you may have notice there are no physical barrier but just a visual indicator.

2.2 Finite State Machine Design

First you need to create the FSM of the car park in order to control it properly.

2.2.1 State Definitions

The following is a possible implementation and is not mandatory.

The system could use five states:

```
type FSM_States is (IDLE, WAIT_PASSWORD, WRONG_PASS, RIGHT_PASS, STOP);
```

2.2.2 State Descriptions

1. **IDLE:** System waiting for a car

- No LEDs active
- Displays off
- Monitors front sensor

2. **WAIT_PASSWORD:** Car detected, waiting for password entry

- Red LED on (steady)

- Display shows “En” (Enter password)
- Waits 10 clock cycles before checking password

3. **WRONG_PASS**: Incorrect password entered

- Red LED blinking
- Display shows “EE” (Error)
- Waits for correct password


4. **RIGHT_PASS**: Correct password, gate opening

- Green LED blinking
- Display shows “GO”
- Monitors sensors for car passage

5. **STOP**: Current car passing, next car detected

- Red LED blinking
- Display shows “SP” (Stop)
- Requires password from next car

2.2.3 State Transition Diagram

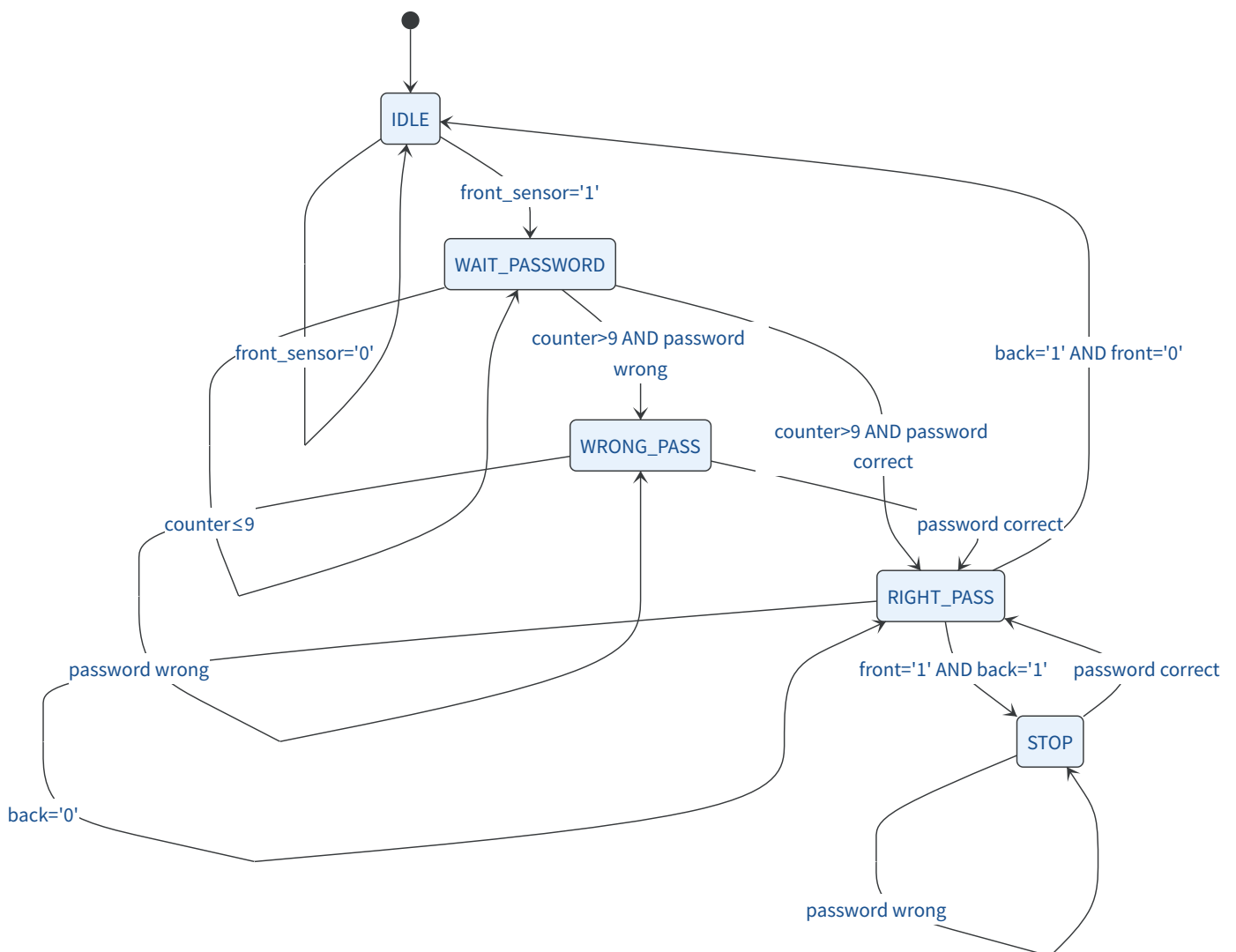

3 Code Implementation

In the following you have some hints on how to proceed. You are not required to follow exactly the same structure.

3.1 Internal Signals

```
signal current_state, next_state: FSM_States;  
signal counter_wait: std_logic_vector(31 downto 0);  
signal red_tmp, green_tmp: std_logic;
```

- `current_state` / `next_state`: FSM state registers
- `counter_wait`: 32-bit counter for password input timing
- `red_tmp` / `green_tmp`: Temporary LED signals for blinking

3.2 Sequential Logic: State Register

```
process(clk, reset_n)  
begin  
    if(reset_n='0') then  
        current_state <= IDLE;  
    elsif(rising_edge(clk)) then  
        current_state <= next_state;  
    end if;  
end process;
```

Purpose: Updates the current state on each clock cycle, with asynchronous reset to IDLE.

3.3 Combinational Logic: Next State Logic

The next state logic is purely combinational and determines state transitions based on:

- Current state
- Sensor inputs
- Password inputs
- Counter value

3.3.1 Key Transition Logic

From IDLE:

```
when IDLE =>  
    if(front_sensor = '1') then  
        next_state <= WAIT_PASSWORD;  
    else  
        next_state <= IDLE;  
    end if;
```

From WAIT_PASSWORD:

```

when WAIT_PASSWORD =>
  if(counter_wait <= x"00000009") then
    next_state <= WAIT_PASSWORD;
  else
    if((password_1="01") and (password_2="10")) then
      next_state <= RIGHT_PASS;
    else
      next_state <= WRONG_PASS;
    end if;
  end if;
end if;

```

From **RIGHT_PASS** (Most Complex):

```

when RIGHT_PASS =>
  if(front_sensor='1' and back_sensor = '1') then
    next_state <= STOP; -- Next car detected while current passing
  elsif(back_sensor= '1') then
    next_state <= IDLE; -- Current car passed, no next car
  else
    next_state <= RIGHT_PASS; -- Gate remains open
  end if;

```

3.4 Counter Process

```

process(clk, reset_n)
begin
  if(reset_n='0') then
    counter_wait <= (others => '0');
  elsif(rising_edge(clk)) then
    if(current_state=WAIT_PASSWORD) then
      counter_wait <= counter_wait + x"00000001";
    else
      counter_wait <= (others => '0');
    end if;
  end if;
end process;

```

Purpose: Creates a 10-clock-cycle delay before checking the password, allowing time for input stabilization.

3.5 Output Process

```

process(clk)
begin
  if(rising_edge(clk)) then
    case(current_state) is
      when IDLE =>
        green_tmp <= '0';
        red_tmp <= '0';
        HEX_1 <= "1111111"; -- off
        HEX_2 <= "1111111"; -- off
      when WAIT_PASSWORD =>
        green_tmp <= '0';


```

```

red_tmp <= '1';
HEX_1 <= "0000110"; -- E
HEX_2 <= "0101011"; -- n
-- ... (other states)
end case;
end if;
end process;

```

3.5.1 7-Segment Display Encoding

 

We will be using a common anode architecture. Therefore in order to light up one of the segments the corresponding pin needs to be put to ground or '0'. So in this logic a '0' is on and a '1' is off.

We can provide some examples of how to encode the different values like:

Character	Segments (gfedcba)	Hex Code	Binary
0	1000000	0x40	Displays "0"
E	0000110	0x06	Displays "E"
n	0101011	0x2B	Displays "n"
P	0001100	0x0C	Displays "P"
S	0100100	0x24	Displays "S"
6	0000010	0x02	Displays "6"

Character	Segments (gfedcba)	Hex Code	Binary
5	0010010	0x12	Displays “5”
Off	1111111	0x7F	All segments off

3.5.2 Output States Summary

State	RED LED	GREEN LED	Display
IDLE	Off	Off	Off
WAIT_PASSWORD	On	Off	“En”
WRONG_PASS	Blinking	Off	“EE”
RIGHT_PASS	Off	Blinking	“GO”
STOP	Blinking	Off	“SP”

4 Design Considerations

4.1 Timing Analysis

1. **Password Check Delay:** The system waits for 10 clock cycles (`counter_wait <= 9`) before validating the password. This provides setup time for password inputs.
2. **LED Blinking:** LEDs toggle on every clock edge in their respective states. The blink frequency equals the clock frequency.

4.2 Sensor Logic

- The system uses two sensors to detect car position:
- **Front sensor only:** Car approaching → Enter password
 - **Back sensor only:** Car passed through → Return to IDLE
 - **Both sensors:** Current car passing + next car waiting → STOP state
- This prevents multiple cars from entering without proper authentication.

5 Testing Strategy

5.1 Test Scenarios

- You need to create the testbenches to validate the following scenarios:
- 5.1.1 Scenario 1: Normal Entry

1. Assert `front_sensor = '1'`
2. Wait 10+ clock cycles
3. Input correct password: `password_1 = "01"`, `password_2 = "10"`
4. Verify: GREEN LED blinks, display shows "GO"
5. Assert `back_sensor = '1'`
6. Verify: System returns to IDLE

5.1.2 Scenario 2: Wrong Password

1. Assert `front_sensor = '1'`
2. Wait 10+ clock cycles
3. Input wrong password: e.g., `password_1 = "00"`, `password_2 = "00"`
4. Verify: RED LED blinks, display shows "EE"
5. Input correct password
6. Verify: System transitions to RIGHT_PASS

5.1.3 Scenario 3: Multiple Cars

1. Car 1 enters with correct password → RIGHT_PASS
2. Before `back_sensor = '1'`, assert `front_sensor = '1'` again
3. Verify: System enters STOP state
4. Input correct password for car 2
5. Verify: Both cars processed correctly

5.1.4 Scenario 4: Reset

1. Put system in any state
2. Assert `reset_n = '0'`
3. Verify: System immediately returns to IDLE
4. All outputs reset

5.2 Testbench Development

You will develop a VHDL testbench to verify these scenarios. Your testbench should:

1. Instantiate the `Car_Parking_System_VHDL` entity
2. Generate a clock signal (suggested period: 20 ns for 50 MHz)
3. Apply reset at simulation start
4. Create stimulus for all test scenarios
5. Monitor and verify outputs
6. Use assertions or report statements for automated checking

5.2.1 Suggested Testbench Structure

```
-- Entity with no ports (testbench)
entity tb_car_parking is
end tb_car_parking;

architecture testbench of tb_car_parking is
-- Component declaration
```



```

component Car_Parking_System_VHDL is
  port (
    -- ports here
  );
end component;

-- Test signals
signal clk_tb : std_logic := '0';
signal reset_n_tb : std_logic := '0';
-- ... other signals

-- Clock period
constant clk_period : time := 20 ns;

begin
  -- Clock generation
  clk_tb <= not clk_tb after clk_period/2;

  -- DUT instantiation
  DUT: Car_Parking_System_VHDL
    port map (
      clk => clk_tb,
      -- ... other port maps
    );

  -- Stimulus process
  stimulus: process
  begin
    -- Test scenarios here
    wait;
  end process;

end testbench;

```

6 Exercises

1. Once you have something that is working ask other groups for their testbenches and confront your implementations and results.
2. Add an extra state called **TIMEOUT** that activates if password isn't entered within 10 clock cycles. think of what should happen and how to handle it.
3. Implement a prescaler to make LEDs blink at 1 Hz instead of at clock frequency.
4. Add a **car_count** output that tracks how many cars have entered.

7 Simulation and Analysis

7.1 Using GHDL

You are asked to create your vhdl code and test it using GHDL.

```
#####
#  GHDL HELP                                     #
#                                                                 #
#  -a [OPTS] FILES      Analyze FILES             #
#  -e [OPTS] UNIT [ARCH] Elaborate UNIT           #
#  -r,--elab-run [OPTS] UNIT [ARCH] [RUNOPTS] Run UNIT #
#  -c [OPTS] FILES -r UNIT [ARCH] [RUNOPTS] Compile, elaborate and run UNIT#
#  -m [OPTS] UNIT [ARCH] Make UNIT                #
#  --gen-makefile [OPTS] UNIT [ARCH] Generate a Makefile for UNIT #
#  --disconfig          Disp tools path           #
#  --run-help           Disp help for RUNOPTS options #
#  -i [OPTS] FILES      Import units of FILES     #
#  -s [OPTS] FILES      Check syntax of FILES     #
#  -d or --dir          Disp contents of the work library #
#  -f FILES             Disp units in FILES       #
#  --clean              Remove generated files    #
#  --remove             Remove generated files and library file #
#  --copy               Copy work library to current directory #
#  --disp-standard      Disp std.standard in pseudo-vhdl #
#  --chop [OPTS] FILES  Chop FILES               #
#  --lines FILES        Precede line with its number #
#  --pp-html FILES      Pretty-print FILES in HTML #
#  --xref-html FILES    Display FILES in HTML with xrefs #
#  --xref FILES         Generate xrefs            #
#  -h or --help [CMD] Disp this help or [help on CMD] #
#  -v or --version      Disp ghdl version         #
#  --options-help       Disp help for analyzer options #
#####
#  To display the options of a GHDL program,      #
#  run your program with the --help option.      #
#  Also see --options-help for analyzer options. #
#####
```

For Windows users:

remember to add your ghdl.exe in the path or use:

```
Set-Alias -Name ghdl -Value C:\...\your path\ghdl.exe
```

7.1.1 Compilation Steps

```
#analyzes your file and let you know if there are issues
```

```
ghdl -a YOUR_DESIGN.vhd
```

```
#compiles both files and generates object: work-obj93.cf
```

```
ghdl -c YOUR_TESTBENCH.vhd YOUR_DESIGN.vhd
```

```
# [OPTIONAL] displays the entity and architectures compiled
```

```
ghdl -d
```

7.1.2 Simulation Execution

The first thing you need to do is guess the length needed to test your design and replace it with the appropriate value in XXXXX.

```
ghdl -r YOUR_TESTBENCH_ENTITY --vcd=NAME_OF_SIMULTION.vcd --stop-time=XXXXXms

#execute the testbench ENTITY and output all the signals into the file NAME_OF_SIMULTION.vcd
#and stops after XXXXXms if the simulation has not finished before
```

Pay attention that you must use the entity created in the previous step and not the vhd file.

You might need to repeat the compile several times before getting a working simulation.

7.1.3 Waveform Viewing

You can use GTKWAVE or the VAPORVIEW extension in VsCode.

8 Conclusion

This car parking system demonstrates practical FSM design principles:

- **Clear state definition** with distinct behaviors
- **Robust sensor handling** to manage multiple cars
- **User feedback** through LEDs and displays
- **Security** via password validation

The design is synthesizable and can be implemented on FPGA development boards with appropriate I/O mapping.

9 References

- IEEE Standard VHDL Language Reference Manual (IEEE Std 1076)
- FPGA Prototyping by VHDL Examples - Pong P. Chu
- Digital Design - M. Morris Man, Michael D. Ciletti

9.1 Potential Improvements (for a future implementation)

You can suggest some improvements of your own

1. **Blink Rate Control:** Add a prescaler to slow down LED blinking for visual clarity
2. **Password Attempts:** Limit wrong password attempts
3. **Timeout:** Add timeout in WAIT_PASSWORD state
4. **Debouncing:** Add debounce logic for sensor inputs
5. **Variable Password:** Make password programmable rather than hardcoded